








# LKS2 - Spring 1 - Electricity


Key Vocabulary		Components (Parts) Vocabulary		
<b>electricity</b>	The flow of an electric current through a material, e.g. from a power source through wires to an <b>appliance</b> .	<b>cell:</b> Normally, we would call this a <b>battery</b> but scientifically, this is a cell. Two or more cells joined together form a <b>battery</b> .	<b>bulb:</b> Lights up in a complete <b>circuit</b> .	<b>buzzer:</b> Makes a noise in a complete <b>circuit</b> .
<b>appliances</b>	A piece of equipment or a device designed to perform a particular job, such as a washing machine or mobile phone.			
<b>battery</b>	A device that stores electrical energy as a chemical.	<b>wires:</b> Used to connect the different components in the <b>circuit</b> together.	<b>motor:</b> Produces movement in a complete <b>circuit</b> .	<b>switch:</b> Used to turn other components in the <b>circuit</b> on or off.
<b>circuit</b>	A pathway that <b>electricity</b> can flow around. It is based around wires and a power supply. Examples of components (parts) you can add in to a <b>circuit</b> are bulbs, switches, buzzers and motors.			

**Complete Circuit**

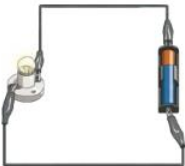


**Electricity** can flow. The components will work.

**Incomplete Circuit**




There is a break in the **circuit** that prevents the **electricity** from flowing. The components will not work.


Switches can be used to open or close a **circuit**. When off, a switch 'breaks' the **circuit** to stop the flow of **electricity**. When on, a switch 'completes' the **circuit** and allows the **electricity** to flow.





toggle switch



push button switch




slide switch

Key Vocabulary		Key Knowledge	
<b>mains electricity</b>	<b>Electricity</b> supplied through wires to a building.	<b>Examples of Electrical Conductors</b>	<b>Examples of Electrical Insulators</b>
<b>electrical conductor</b>	A <b>conductor</b> of <b>electricity</b> is a material that will allow <b>electricity</b> to flow through it.	 water   metal	 wood   plastic paper   rubber   glass   fabric
<b>electrical insulator</b>	Materials that are <b>electrical insulators</b> do not allow <b>electricity</b> to flow through them.		


**Appliances**

Many everyday **appliances** rely on **electricity** for them to work. Some **appliances** use **mains electricity** (are plugged into a socket) and others have a **battery** to make them work. Examples of **mains**-powered **appliances** include toasters and televisions. **Battery**-powered **appliances** can include mobile phones and torches.

**mains-powered**




**battery-powered**




To work safely with **circuit** components in the classroom:

- None of the equipment needs to use mains power, so do not put any of it in or near plugs.
- Report any damaged or broken equipment to your teacher. Do not use it.
- Only use equipment as instructed.
- Connect equipment correctly.
- Disconnect equipment after use and put it away neatly.


Materials can be tested in a **circuit** to see if they are **electrical conductors** or **electrical insulators**.



10p = metal =  
**electrical conductors**



test **circuit**



ruler = plastic =  
**electrical insulators**